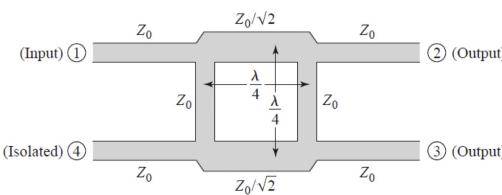



打底




A branch-line coupler

Use even & odd mode analysis.

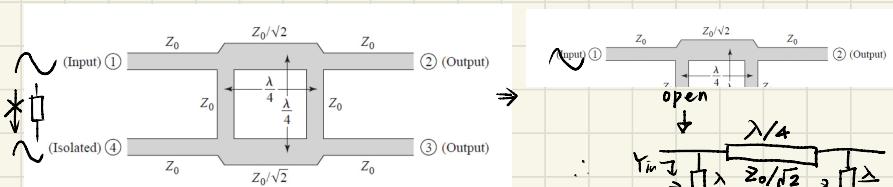① Let mode coming in from the left ports that are in-phase, which is even, we have virtual open.




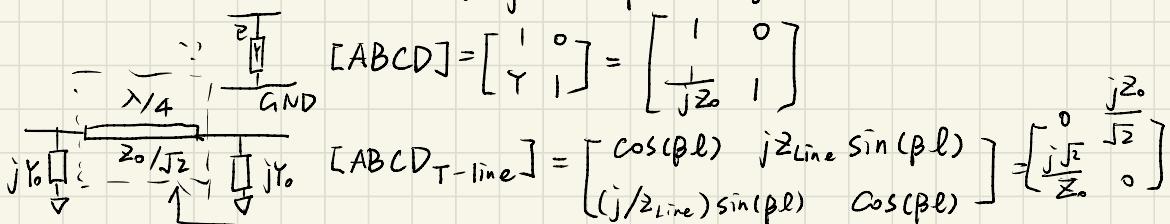
$$ABCD \text{ Analysis: } Z_{in} = Z_0 \left( \frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)} \right) = \frac{Z_0}{j} \quad Y_{in} = \frac{j}{Z_0} = jY_0$$



$$\therefore [ABCD] = \begin{bmatrix} 1 & 0 \\ \frac{1}{jZ_0} & 1 \end{bmatrix} \begin{bmatrix} 0 & \frac{jZ_0}{\sqrt{2}} \\ \frac{j\sqrt{2}}{Z_0} & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ \frac{1}{jZ_0} & 1 \end{bmatrix}$$

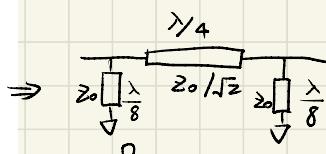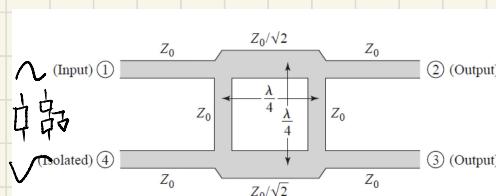② let an in-phase signal on one port, and an out-of-phase signal on the other port, we have a virtual ground.




$$ABCD \text{ Analysis: } Z_{in} = Z_0 \left( \frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)} \right) = jZ_0, \quad Y_{in} = \frac{1}{jZ_0} = -jY_0$$

$$\therefore [ABCD] = \begin{bmatrix} 1 & 0 \\ -\frac{1}{j\sqrt{2}} & 1 \end{bmatrix} \begin{bmatrix} 0 & \frac{1}{j\sqrt{2}} \\ \frac{j}{\sqrt{2}} & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ -\frac{1}{j\sqrt{2}} & 1 \end{bmatrix}$$

Use Table from Polar to convert to S-parameter

$$\begin{array}{c} \text{Table} \\ \text{Even} \\ \text{Odd} \end{array} \quad S_E^o = \begin{bmatrix} 0 & \frac{-1-j}{j\sqrt{2}} \\ \frac{-1-j}{j\sqrt{2}} & 0 \end{bmatrix} \quad + \text{Even} \\ - \text{odd}$$

Put it all together

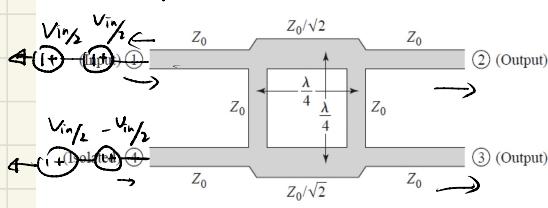

$$S_{11} = S_{22} = S_{33} = S_{44} = 0$$

$$S_{31} = \left. \frac{V_3^-}{V_1^+} \right|_{a_2=a_3=a_4=0} = \frac{V_3^{-e} + V_3^{-o}}{V^+ + V^+} = \frac{1}{2} \left( \frac{V_3^{-e}}{V^+} + \frac{V_3^{-o}}{V^+} \right) = \frac{1}{2} \left( \frac{V_2^-}{V^+} - \frac{V_2^+}{V^+} \right) = \frac{1}{2} (S_{21}^e - S_{21}^o) = \frac{1}{2} \left[ \left( \frac{-1-j}{j\sqrt{2}} \right) - \left( \frac{1-j}{j\sqrt{2}} \right) \right] = -\frac{1}{j\sqrt{2}}$$

$$S_{31} = S_{13} = S_{42} = S_{24} = -\frac{1}{j\sqrt{2}}$$

$$S_{41} = \left. \frac{V_4^-}{V_1^+} \right|_{a_2=a_3=a_4=0} = \frac{V_4^{-e} + V_4^{-o}}{V^+ + V^+} = \frac{V_4^{-e} + V_4^{-o}}{2V^+} = \frac{V_1^{-e} - V_1^{-o}}{2V^+} = \frac{1}{2} (S_{11}^e - S_{11}^o) = 0$$

$$S_{41} = S_{14} = S_{32} = S_{23} = 0$$

$$\therefore [S] = -\frac{1}{j\sqrt{2}} \begin{bmatrix} 0 & j & 1 & 0 \\ j & 0 & 0 & 1 \\ 1 & 0 & 0 & j \\ 0 & 1 & j & 0 \end{bmatrix} \quad (S_{12} \text{ has a } 90^\circ \text{ phase shift compared to } S_{13})$$